

Total Pages—2

**C/21/BCA/1st Seme/1197(set-1)**

**2020**

**BCA**

**1st Semester Examination**

**DIGITAL ELECTRONICS LAB**

**PAPER—1197 (Set-I)**

**(PRACTICAL)**

*Full Marks : 100*

*Time : 3 Hours*

*The figures in the right-hand margin indicate full marks.*

*Candidates are required to give their answers in their own words as far as practicable.*

*Answer any two questions taking one from each group*

**Group A**

35×1

1. Design a full adder using NAND gates and verify its truth table.

*(Turn Over)*

2. Design gray code to BCD converter and verify the truth table.
3. Design a 1:4 DEMUX and verify its truth table.
4. Design a 3 to 8 decoder and verify the truth table.

**Group B**

35×1

5. Design a 4-bit ripple counter using J-K flip-flop.
6. Design an asynchronous up counter of MOD 5.
7. Design and implement a right shift register and verify the operation.
8. Design a 4-bit bidirectional shift register.

**[ Internal Assessment : 30 ]**

*INSTRUCTIONS*

1. Problem Definition	:	3 Marks
2. Circuit Diagram	:	15 Marks
3. Truth Table	:	12 Marks
4. Output / Result with discussion	:	5 Marks
Total	:	35 Marks